

SRI SIDDHARTHA INSTITUTE OF TECHNOLOGY, TUMAKURU

(A constituent college of Sri Siddhartha Academy of Higher Education, Tumakuru)

CS3TH5: Digital Circuit Design & Applications

Time: 1 Hr

Date: 27/11/2021

TEST 1

Max Marks: 30

Answer all the questions

- | | M | C | B |
|---|---|---|---|
| 1 | 6 | 1 | 2 |
| What are Maxterms? Convert the given Boolean expression to standard POS and later to Maxterm Canonical form | | | |
| (ii) $f(abc) = (\bar{a} + c) \cdot (b + c)$ (ii) $f(abc) = \bar{c}$ | | | |
| 2 | 6 | 2 | 3 |
| Design one bit comparator using basic gates and NAND gates. | | | |
| 3 | 6 | 4 | 5 |
| Write the Verilog code for the logic circuit which produces logic-1 output for even number of 1's for the set of 8 input combinations. | | | |
| 4 | 6 | 2 | 3 |
| Design a Combinational logic circuit which accepts four input variables and produces logic-0 output for those input combinations which have two or more zeros. Use Minimum number of logic gates. | | | |
| 5 | 6 | 2 | 4 |
| Simplify the following expressions using K-map | | | |
| (iii) $f(abcd) = \sum m(1, 3, 4, 6, 10, 11, 15)$ | | | |
| (iv) $y(pqrs) = \pi M(0, 2, 5, 6, 8, 9, 12, 14,)$ | | | |
| Write the logic circuit for the simplified expression using universal gates | | | |

NOTE: M - Marks, C - Course Outcome and B - Bloom's level

SRI SIDDHARTHA INSTITUTE OF TECHNOLOGY, TUMAKURU

(A constituent college of Sri Siddhartha Academy of Higher Education, Tumakuru)

CS3TH5: Digital Circuit Design & Applications

Date:01/01/2022

TEST 2

Time:1Hr

Answer all the questions }

Max Marks: 30

- | | M | C | B |
|---|---|-----|-----|
| 1 Design Adder / Subtractor circuit using 4 bit adder IC 7483 and write the single truth table to depict the addition and subtraction of following numbers.
(iv) A=6 & B= 2
(v) A=7 & B=5
(vi) A=4 & B=1 | 6 | 2 | 6 |
| 2 Write the HDL code for 3:8 Decoder using Case statement | 6 | 4 | 3 |
| 3 Realize the given Boolean Expression using suitable Multiplexer
$F(ABCD) = \sum m(0,1,2,4,6,8,9,11,12,14,15)$
$P(XYZ) = \prod M(1,3,4,6)$ | 6 | 2,3 | 4,6 |
| 4 Write the Truth Table of BCD to 7 Segment decoder and obtain the Boolean expression for the segment 'd' | 6 | 2 | 5 |
| 5 Design a logic circuit which converts 2^3 decimal inputs to 3 bit Binary output | 6 | 1,2 | 5,6 |

NOTE: M-Marks, C- Course Outcome and B – Bloom's level

SRI SIDDHARTHA INSTITUTE OF TECHNOLOGY, TUMAKURU

(A constituent college of Sri Siddhartha Academy of Higher Education, Tumakuru)

CS3TH5: Digital Circuit Design & Applications

Date:05/02/2022

TEST - 3

Time:1Hr

Answer all the questions

Max Marks: 20

		M	CO	BL
1	Explain the working of D Flip Flop and mention the merits of D Flip Flop	5	1	2
2	Obtain the characteristic equation of SR and JK Flip Flop	5	2	5
3	Convert SR flip flop to D Flip Flop	5	2,3	6
4	Design Mod 4 Synchronous up counter and write the Timing diagram	5	2	4

NOTE: M -Marks, C- Course Outcome and B – Bloom's level